

$$\eta = \frac{S \times P.F.}{S \times P.F. + P_i + P_{cu}}$$

Sheet


1 ϕ - Transformer, 220 / 240 V, 50 Hz
 $R_{ie} = 0.02 \Omega$, $X_{ie} = 0.2 \Omega$

O.C. Test \Rightarrow 220 V, 1.8 A, 39.6 W

Load \Rightarrow 3 kW, 0.8 lag, 240 V

Req: R%, η

$$\phi = \cos^{-1} 0.8 = 36.87^\circ$$

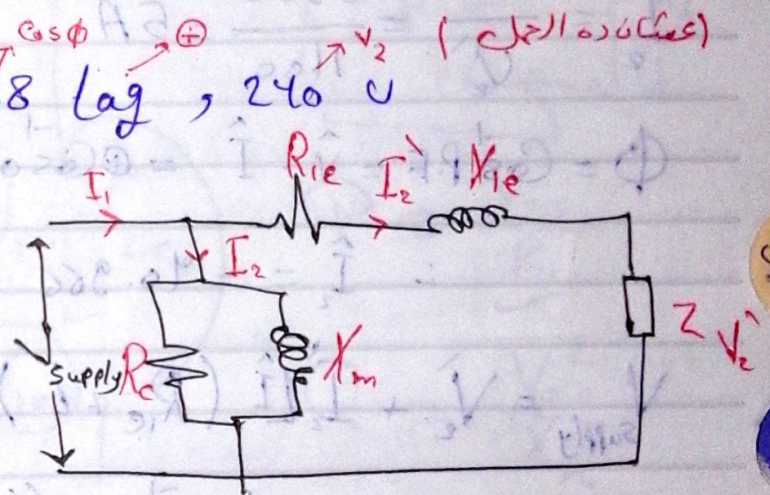

$$P_{load} = V_2 I_2' \cos \phi$$

$$3000 = 240 \times I_2' \times 0.8 \Rightarrow I_2' = 15.625 \text{ A}$$

$$R\% = \frac{I_2' R_{ie} \cos \phi + I_2' X_{ie} \sin \phi}{V_1} = \dots$$

$$36.8 \leftarrow \frac{13}{2} \times 0.8$$

[2] 1100/110 V step down 1- ϕ transformer

$$R_c = 2 \text{ k}\Omega, X_m = 1.5 \text{ k}\Omega, R_1 = 4 \Omega, X_1 = 3 \Omega$$

$$R_2 = 0.04 \Omega, X_2 = 0.03 \Omega$$

Load \Rightarrow 5.5 kVA, 0.8 lag, 110 V

Req: $V_{\text{supply}}, R\%, \eta\%$

$$\hat{I}_2 = \frac{S}{V_2} = \frac{5500}{110} = 5 \text{ A}$$

$$\Phi = \cos^{-1} \text{P.F.} = \hat{V} - \hat{I} = \cos^{-1} 0.8 = \hat{0} - \hat{I}$$

$$\hat{I}_2 = -40.96^\circ = -\cos^{-1} 0.8$$

$$V_{\text{supply}} = V_2 + \hat{I}_2 \hat{I} (R_{1e} + jX_{1e})$$

$$= 1100 + 5 \angle -\cos^{-1} 0.8 \left(\frac{4+4}{2} + j \frac{3+3}{2} \right)$$

$$= 1100 + 2(16 + j9) = 1150$$

$$P_i = \frac{V_{\text{supply}}^2}{R_c} \quad \text{approximate} \quad P_i = \frac{1150^2}{2000} = 661.25 \text{ watt}$$



$$\eta = \frac{\hat{I}_2 V_2 \cos \phi}{\hat{I}_2 V_2 \cos \phi + P_i + \hat{I}_2^2 (R_{1e})} = \frac{5 \times 1100 \times 0.8}{5 \times 1100 \times 0.8 + 661.25 + 5^2 \times 8} = 83.63\%$$

5] 5 KVA, 500/250 V, 50 Hz, 1 ϕ - Transformer

O.C. Test \Rightarrow 500 V, 1 A, 50 W (L.V side open) $\xrightarrow{P_i}$

S.C. Test \Rightarrow 25 V, 10 A, 60 W (L.V side shorted)

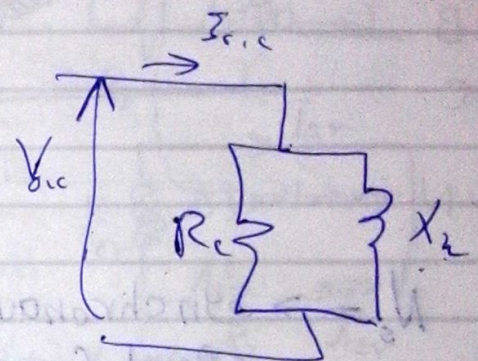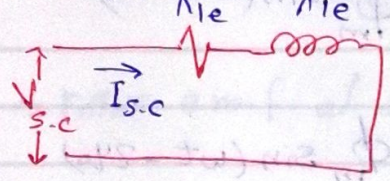Req. η %; R_e %; η %
 F.L 0.8 lag R_{ie} X_{ie} η 60% FL 0.8 lead



$$P = I_{sc}^2 R_{ie}, S = V_{sc} \times I_{sc}$$

$$P = \frac{V_{oc}^2}{R_e}$$

$$Q = \sqrt{S^2 - P^2} = I_{sc}^2 X_{ie}$$


$$Q = \frac{V_{oc}^2}{X_e}$$

$$S = V_{oc} \times I_{sc}$$

^ - ^ transformer circuit diagram

Data:- 10 kVA, 220/110V transformer
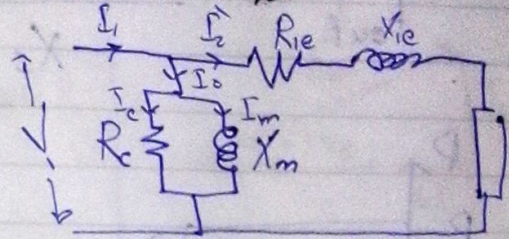
$$\begin{aligned} R_1 &= 0.02 \Omega & X_1 &= 0.04 \Omega \\ R_2 &= 0.01 \Omega & X_2 &= 0.01 \Omega \\ R_c &= 200 \Omega & X_m &= 300 \Omega \end{aligned}$$



if the transformer is supplying 75% of its full load at unity Power Factor & rated secondary voltage find

- The transformer referred circuit Parameters
- The voltage regulation
- The transformer efficiency

$$R_{1e} = R_1 + R_2' = R_1 + R_2/k^2 ; k = \frac{V_2}{V_1} = \frac{110}{220} = 0.5$$

$$= 0.02 + \frac{0.01}{0.5^2} = 0.06 \Omega$$

$$X_{1e} = X_1 + X_2' = 0.04 + \frac{0.01}{0.5^2} = 0.08 \Omega$$

$$R_{2e} = R_2 + k^2 R_1 = 0.01 + 0.5^2 \times 0.02 = 0.015 \Omega$$

$$X_{2e} = X_2 + k^2 X_1 = 0.01 + 0.04 \times 0.5^2 = 0.02 \Omega$$

at F.L :- $I_1 = \frac{10 \times 10^3}{220} = 45.45 \text{ A}$

~~$I_2 = \frac{10 \times 10^3}{110} = 90.91 \text{ A}$~~

$$I_c = \frac{V_1}{R_c} = \frac{220}{200} = 1.1 \text{ A}, I_m = \frac{V_1}{X_m} = \frac{220}{300} = 0.667 \text{ A}$$

$$\cancel{I_2} = I_1 = I_0 = 45.45$$

$$P_i = I_c^2 R_c = 1.1^2 \times 200 = 242 \text{ watt}$$

$$P_{cu} = I_2^2 R_{le} = 45.45^2 \times 0.06 = 124 \text{ watt}$$

$$\eta = \frac{n V_2 I_2 \cos \phi}{n V_2 I_2 \cos \phi + P_i + P_{cu}} = \frac{220 \times 45.45 \times 1 \times 0.75}{0.75 \times 220 \times 45.45 + 242 + 0.75^2 \times 124} \times 100$$

$$\eta = 96 \%$$

$$R = \frac{I_1 R_{le} \cos \phi + I_1 X_{le} \sin \phi}{V_1}$$

$$= \frac{45.45 \times 0.06}{220} \times 100 = 1.24 \%$$